

Phasor solution (steady state)

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$

$$\tilde{I}(z) = I_0^+ e^{-\gamma z} + I_0^- e^{+\gamma z}$$

from telegrapher's equations

$$\begin{matrix} \uparrow \\ V_0^+ \\ \hline Z_0 \end{matrix}$$


$$\begin{matrix} \uparrow \\ -V_0^- \\ \hline Z_0 \end{matrix}$$

sol. to wave eqn derived from telegrapher's eqns Urban

$$\text{with } Z_0 = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}}$$

$$\text{and } \gamma = \sqrt{(R' + j\omega L')(G' + j\omega C')}$$

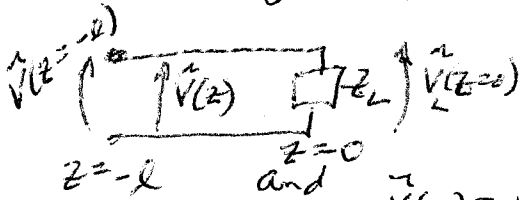by setting $Z_L = \frac{\tilde{V}_L(z=0)}{\tilde{I}_L(z=0)}$, find $\frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0} \equiv \Gamma_V$



thus $\tilde{V}(z) = V_0^+ (e^{-\gamma z} + \Gamma_V e^{+\gamma z})$

$$\tilde{I}(z) = \frac{V_0^+}{Z_0} (e^{-\gamma z} - \Gamma_V e^{+\gamma z})$$

$$\frac{I_0^-}{I_0^+} = -\Gamma_V$$


for lossless case ($R' = G' = 0$)

$$\tilde{V}(z) = V_0^+ (e^{-j\beta z} + \Gamma_V e^{+j\beta z})$$

$$\tilde{I}(z) = \frac{V_0^+}{Z_0} (e^{-j\beta z} - \Gamma_V e^{+j\beta z})$$

$$\text{with } Z_0 = \sqrt{\frac{L'}{C'}}; \beta = \omega \sqrt{LC'}$$
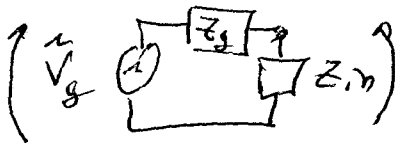
$$Z_{in}(-l) = \frac{\tilde{V}(z=-l)}{\tilde{I}(z=-l)} = Z_0 \left(\frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \right)$$



smaller-hand

$$\tilde{V}_i(z=-l) = \frac{V_g Z_{in}}{Z_g + Z_{in}}$$

$$\tilde{V}_i(z=-l) = V_0^+ (e^{+j\beta l} + \Gamma_V e^{-j\beta l})$$

$$V_0^+ = \left(\frac{V_g Z_{in}}{Z_g + Z_{in}} \right) \left(\frac{1}{e^{+j\beta l} + \Gamma_V e^{-j\beta l}} \right)$$





$$\Gamma_V = |\Gamma_V| e^{j\theta_r}$$

$$\therefore \tilde{V}(z) = \left[\frac{V_g Z_{in}}{Z_g + Z_{in}} \left(\frac{1}{e^{+j\beta l} + \Gamma_V e^{-j\beta l}} \right) \right] \left[e^{-j\beta z} + \Gamma_V e^{+j\beta z} \right]$$

$$\tilde{I}(z) = \left[\left(\frac{V_g Z_{in}}{Z_g + Z_{in}} \right) \left(\frac{1}{e^{+j\beta l} + \Gamma_V e^{-j\beta l}} \right) \right] \left[\frac{1}{Z_0} \right] \left[e^{-j\beta z} - \Gamma_V e^{+j\beta z} \right]$$

St. Wr. Ratio: $S = \frac{1 + |\Gamma_V|}{1 - |\Gamma_V|} = \frac{|V(z)|_{\max}}{|V(z)|_{\min}}; |\tilde{V}(z)| = |V_0^+| \sqrt{1 + |\Gamma_V|^2 + 2|\Gamma_V| \cos(2\beta z + \theta_r)}$

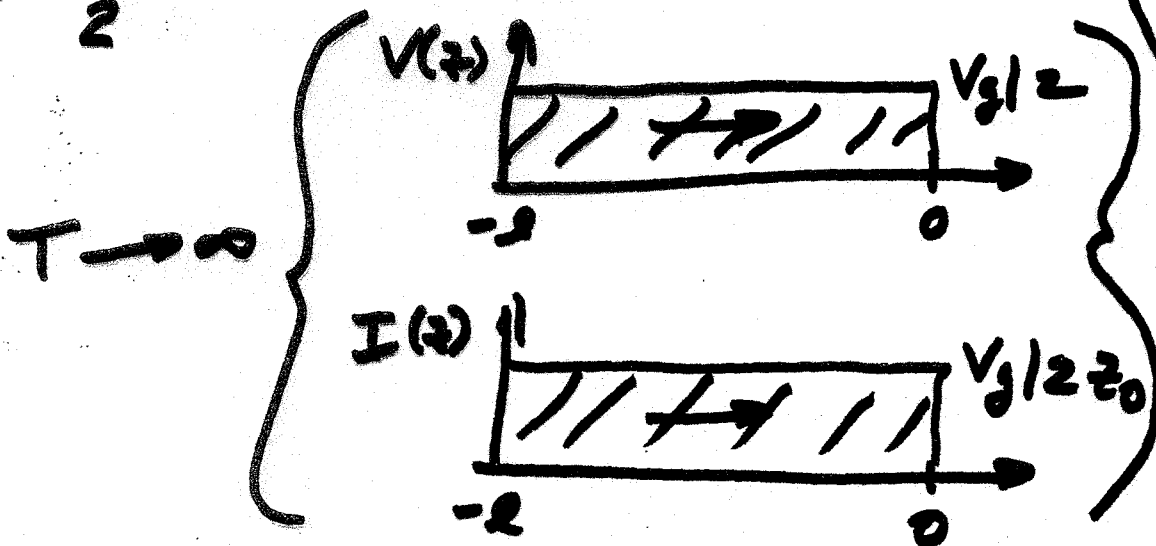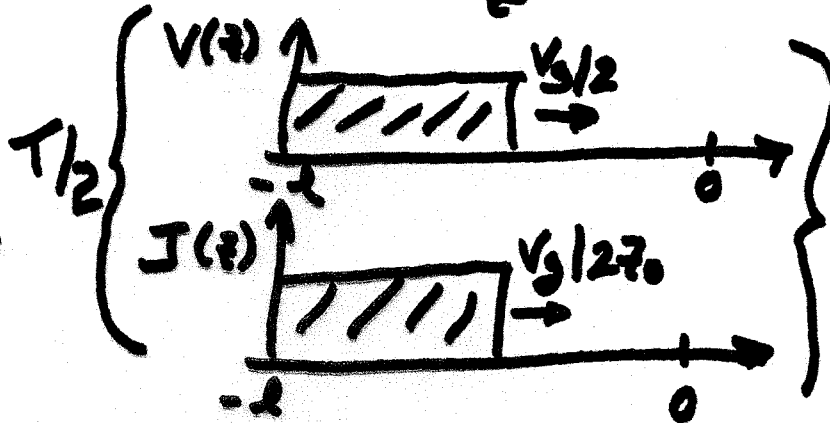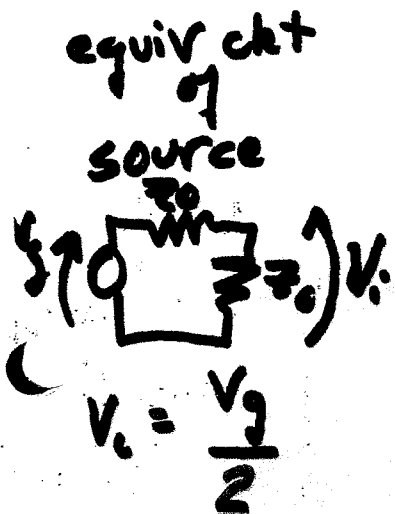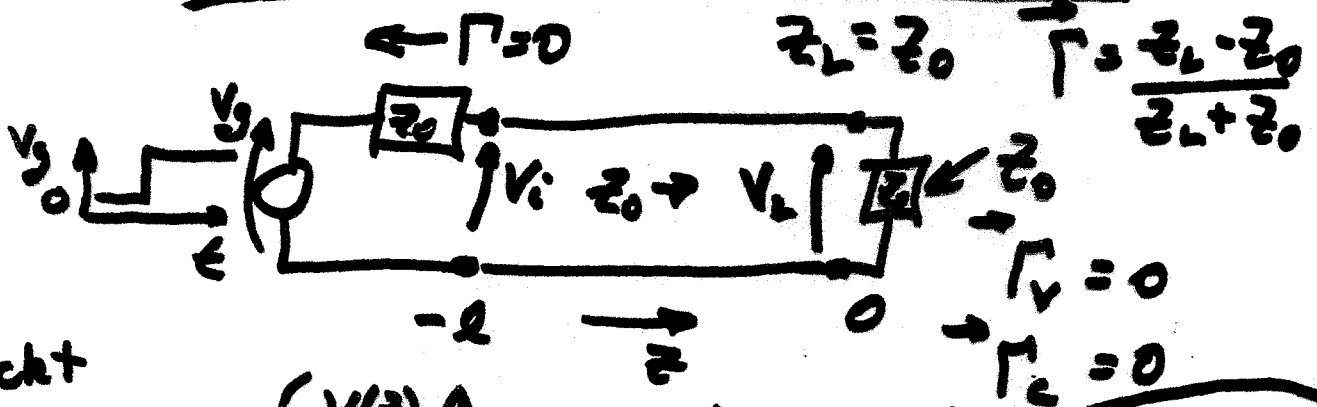
MATCHED LINE WITH STEP FUNCTION INPUT AND LINE CHARACTERISTIC IMPEDANCE Z_0



in d.c. case: $V_L = V_g/2$
 $I_L = V_g/2Z_0$

SHORT CIRCUIT LINE

$\frac{L}{v}$


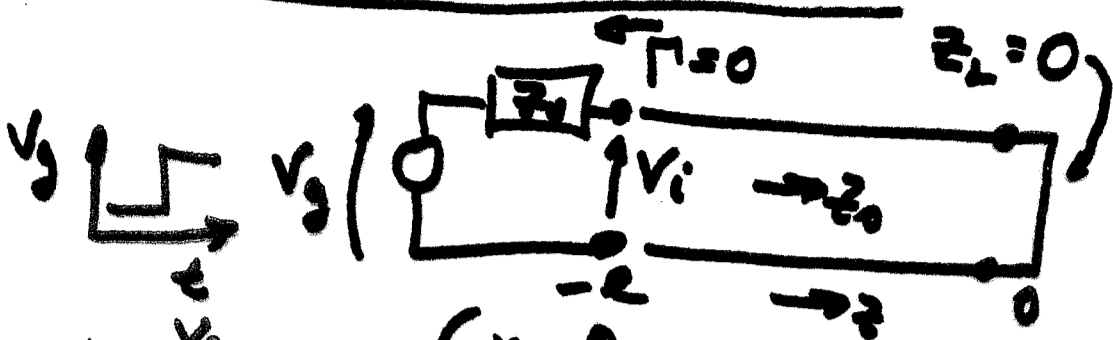


$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Gamma_V = -1$$



$$\Gamma_I = +1$$

$$V_i = \frac{V_g}{2}$$

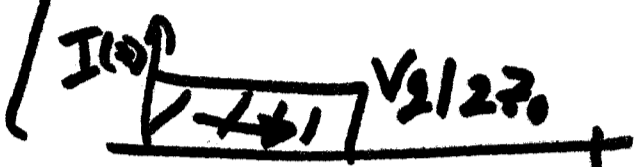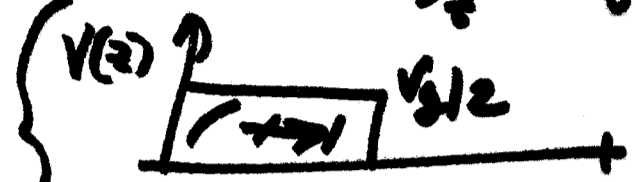

$T/2$

$$T = \frac{L}{v}$$

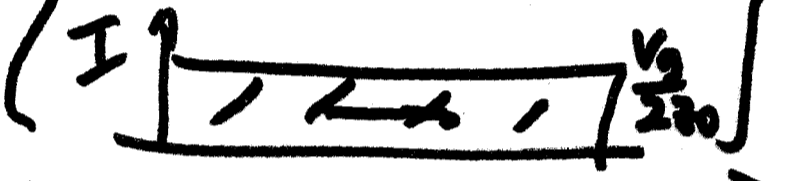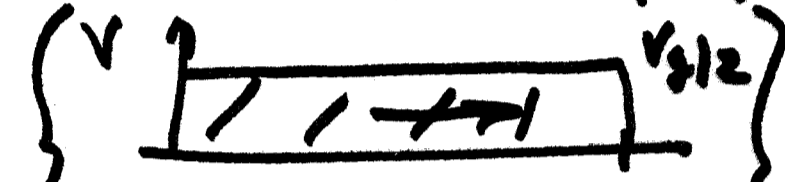



T

$$v = \frac{1}{\sqrt{L'C}}$$


in d.c. case

$$V_L = 0$$

$$I_L = \frac{V_g}{2Z_0}$$

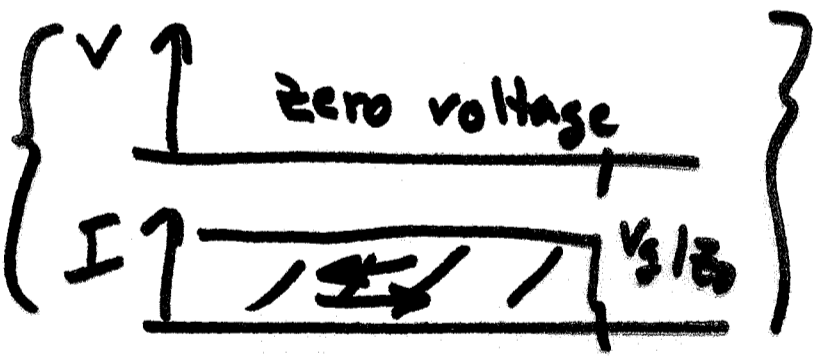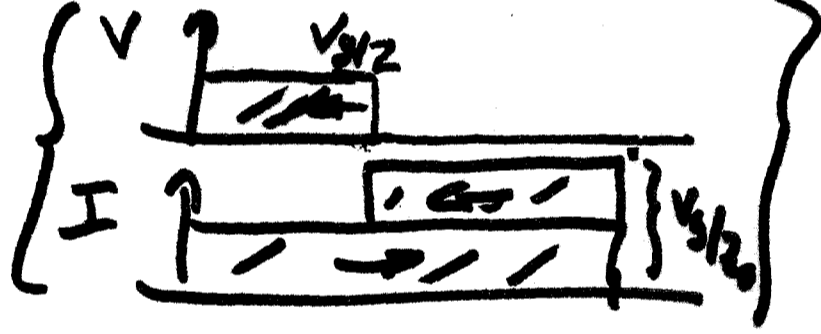


$3T/2$

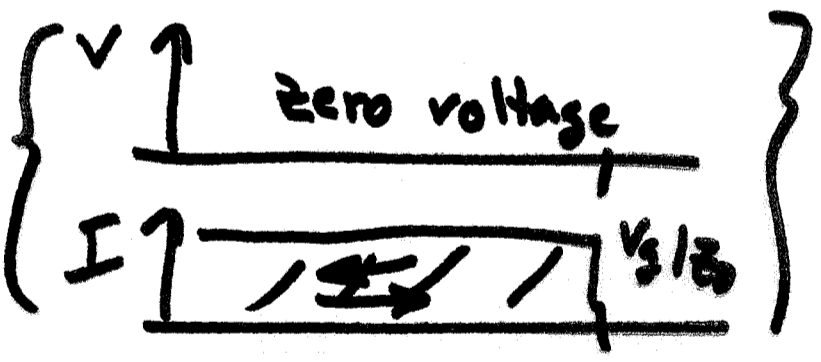

$2T \rightarrow \infty$

OPEN CIRCUIT LINE


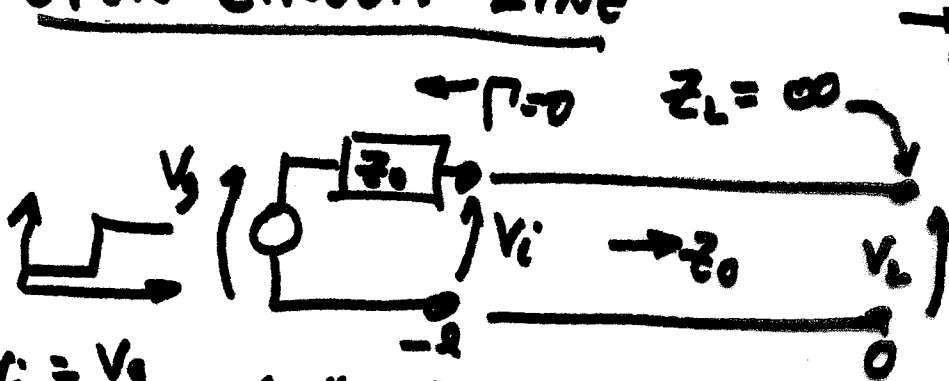


$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$


$$\Gamma_v = +1$$

$$\Gamma_c = -1$$


$$V_i = \frac{V_g}{2}$$

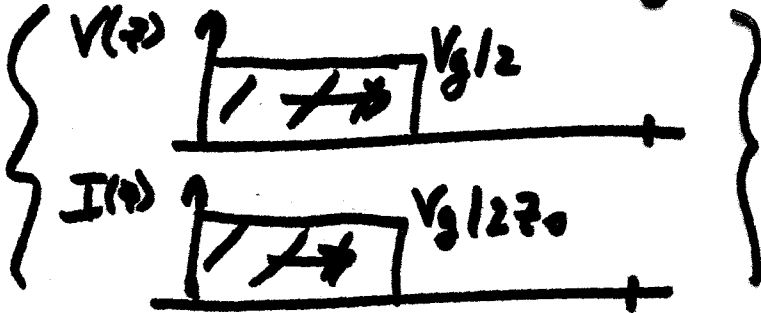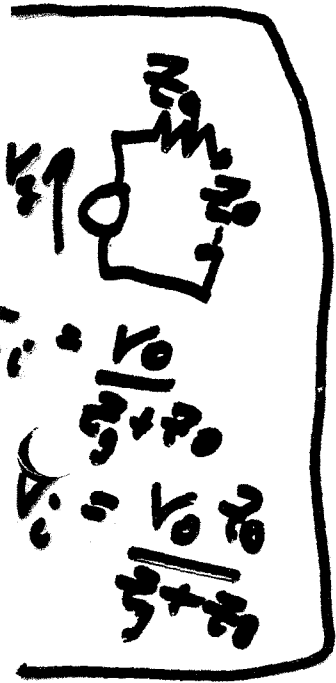

T/2

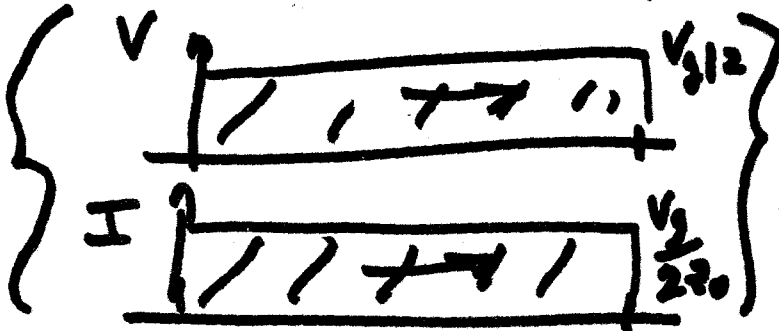

T

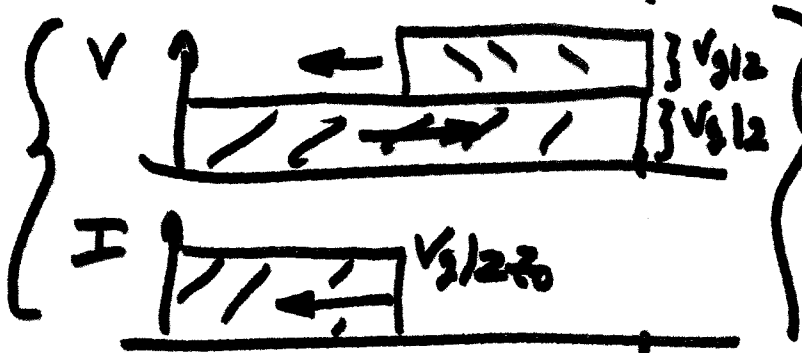

3T/2



2T -> infinity


in d.c. case

$$V_c = V_g$$

$$I_c = 0$$

(also true independent of source impedance, but no bounces)

LINE WITH TERMINATION: $R_L = 3Z_0$ Γ

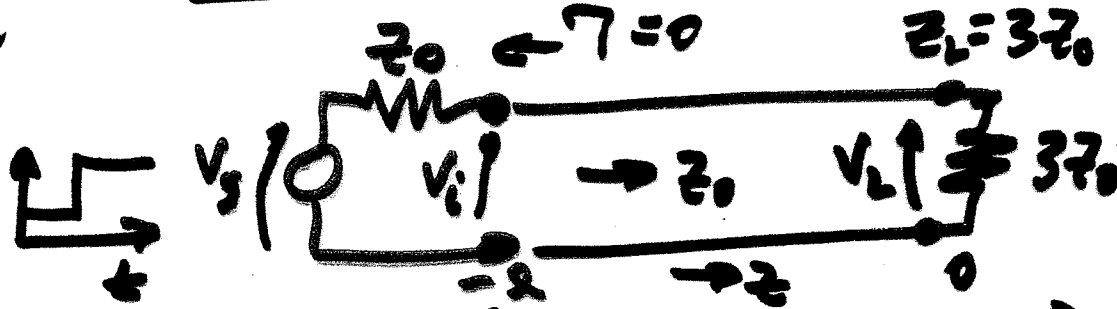


$$\Gamma_v = \frac{3Z_0 - Z_0}{3Z_0 + Z_0}$$

$$\Gamma_v = +1/2$$

$$\Gamma_c = -1/2$$

$$V_i = \frac{V_g}{2}$$

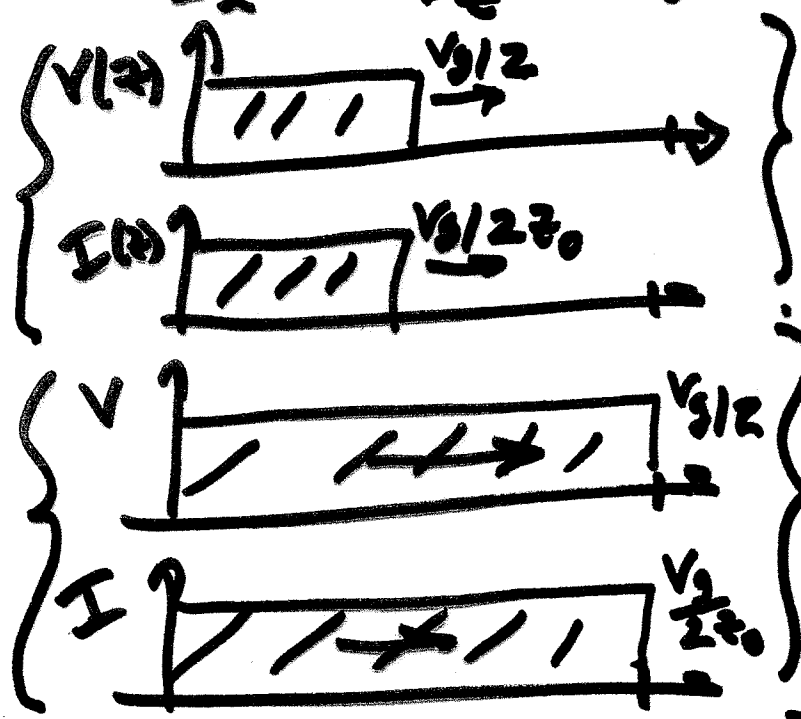

$T/2$

T

$$T = \frac{l}{v}$$


$$v = \frac{1}{\sqrt{LC}}$$

in d.c. case

$$V_L = \frac{3Z_0}{4Z_0} V_g$$

$$= \frac{3}{4} V_g$$

$$I_L = V_g/4Z_0$$

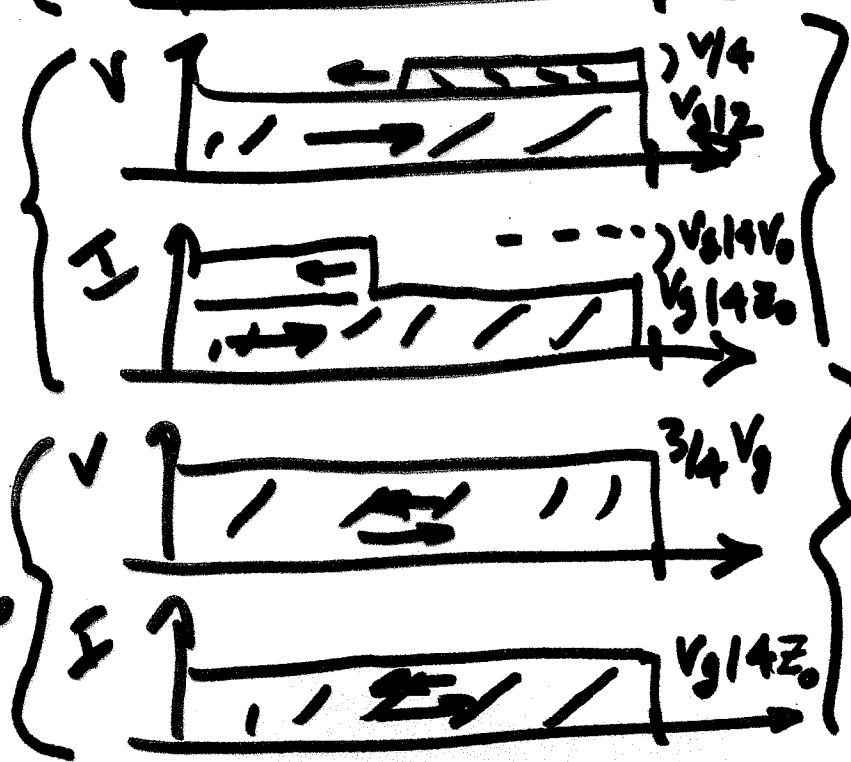

$3T/2$

$2T \rightarrow \infty$