

EEL 3472  
HOMEWORK #3  
DUE FRIDAY, JANUARY 30, 2009

1. Ulaby, page 101. Problem 2.10
2. Ulaby, Page 101, Problem 2.12
3. A voltage generator with  $v_g(t) = A \sin(10^{10}t)$  and internal impedance 10 Ohms is connected to a lossless transmission line characterized by  $L' = 10^{-6} \text{ H/m}$  and  $C' = 10^{-10} \text{ F/m}$ . If the load impedance is 100 Ohms and the line is 10 meters long, find:
  - (a) The phasor voltage source  $\tilde{V}_g$
  - (b) The wave length  $\lambda$  on the line
  - (c) The reflection coefficient at the load
  - (d) The input impedance  $Z_{in}$  to the line
  - (e) The phasor input voltage to the line  $\tilde{V}_i$