

1.

Problem 2.10 Using a slotted line, the voltage on a lossless transmission line was found to have a maximum magnitude of 1.5 V and a minimum magnitude of 0.6 V. Find the magnitude of the load's reflection coefficient.

Solution: From the definition of the Standing Wave Ratio given by Eq. (2.59),

$$S = \frac{|\bar{V}|_{\max}}{|\bar{V}|_{\min}} = \frac{1.5}{0.6} = 2.5 = \frac{1+|\Gamma|}{1-|\Gamma|}$$

Solving for the magnitude of the reflection coefficient in terms of S, as in Example 2.4,

$$|\Gamma| = \frac{S-1}{S+1} = \frac{2.5-1}{2.5+1} = 0.43.$$

$$\begin{aligned} S &= \frac{1+|\Gamma|}{1-|\Gamma|} \\ S-|\Gamma| &= 1+|\Gamma| \\ S-1 &= 2|\Gamma| \\ \frac{S-1}{2} &= |\Gamma| \end{aligned}$$

2.

Problem 2.12 A 50-Ω lossless transmission line is terminated in a load with impedance $Z_L = (30 - j50) \Omega$. The wavelength is 8 cm. Find:

- (a) the reflection coefficient at the load,
- (b) the standing-wave ratio on the line,
- (c) the position of the voltage maximum nearest the load,
- (d) the position of the current maximum nearest the load.

Solution:

(a) From Eq. (2.49a),

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(30 - j50) - 50}{(30 - j50) + 50} = 0.57e^{-j79.8^\circ}$$

(b) From Eq. (2.59),

$$S = \frac{1+|\Gamma|}{1-|\Gamma|} = \frac{1+0.57}{1-0.57} = 3.65.$$

(c) From Eq. (2.56)

$$l_{\max} = \frac{\theta_r \lambda}{4\pi} + \frac{n\lambda}{2} = \frac{-79.8^\circ \times 8 \text{ cm} \pi \text{ rad}}{4\pi \cdot 180^\circ} + \frac{n \times 8 \text{ cm}}{2} = -0.89 \text{ cm} + 4.0 \text{ cm} = 3.11 \text{ cm}.$$

$n = 1, 2 \dots$ if $\theta_r < 0$
 $(\theta_r = -79.8^\circ)$
 $n = 0, 1, 2 \dots$
 if $\theta_r > 0$
 which it is not

(d) A current maximum occurs at a voltage minimum, and from Eq. (2.58),

$$l_{\min} = l_{\max} - \lambda/4 = 3.11 \text{ cm} - 8 \text{ cm}/4 = 1.11 \text{ cm}.$$

Problem 3.

A voltage generator with $v_g(t) = A \sin(10^{10} t)$ and internal impedance 10 Ohms is connected to a lossless transmission line characterized by $L' = 10^{-6} H/m$ and $C' = 10^{-10} F/m$. If the load impedance is 100 Ohms and the line is 10 meters long, find:

- (a) The phasor voltage source \tilde{V}_g
- (b) The wave length λ on the line
- (c) The reflection coefficient at the load
- (d) The input impedance Z_{in} to the line
- (e) The phasor input voltage to the line \tilde{V}_i

$$Z_0 = \sqrt{\frac{L'}{C'}} = \sqrt{\frac{10^{-6}}{10^{-10}}} = 100 \Omega$$

$$u_p = \frac{1}{\sqrt{L'C'}} = \frac{1}{\sqrt{10^{-6} \cdot 10^{-10}}} = 10^8 \text{ m/s}$$

$$\omega = 10^{10} \text{ rad/s} \quad (\frac{1}{3} c)$$

$$f = \frac{10^{10}}{2\pi}$$

$$(a) v_g = A \cos(10^{10} t - \pi/2)$$

$$\tilde{V}_g = A e^{-j\pi/2}$$

$$(b) \lambda = \frac{u_p}{f} = \frac{10^8}{10^{10}/2\pi} = 2\pi \times 10^{-2} \text{ m}$$

$$(c) \Gamma_L = \frac{100 - 100}{100 + 100} = 0$$

(d) Since line is matched at load, $Z_L = Z_0$, $Z_{in} = 100 \Omega$,

or, $Z_{in} = 100 \left[\frac{100 + j100 \tan \beta l}{100 + j100 \tan \beta l} \right] \Omega$

1

$$(e) \tilde{V}_i = \frac{Z_{in}}{Z_{in} + Z_g} \tilde{V}_g$$

\uparrow \uparrow
 100 10

Answers

(a)	$\tilde{V}_g = A e^{-j\pi/2}$
(b)	$\lambda = 2\pi \times 10^{-2} \text{ meters } (\pi/50)$
(c)	$\Gamma_L = 0$
(d)	$Z_{in} = 100 \Omega$
(e)	$\tilde{V}_i = \frac{10}{11} A e^{-j\pi/2}$