

EEL 3472 HW # ~~A~~ SOLUTIONS - FEB 6, 2009

(1)

(4 problems / 4 pages)

#1

Problem 2.21 A voltage generator with $v_g(t) = 5 \cos(2\pi \times 10^9 t)$ V and internal impedance $Z_g = 50 \Omega$ is connected to a $50\text{-}\Omega$ lossless air-spaced transmission line. The line length is 5 cm and it is terminated in a load with impedance $Z_L = (100 - j100) \Omega$. Find

- (a) Γ at the load.
- (b) Z_{in} at the input to the transmission line.
- (c) the input voltage \tilde{V}_i and input current \tilde{I}_i .

Solution:

(a) From Eq. (2.49a),

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(100 - j100) - 50}{(100 - j100) + 50} = 0.62e^{-j29.7^\circ}$$

(b) All formulae for Z_{in} require knowledge of $\beta = \omega/u_p$. Since the line is an air line, $u_p = c$, and from the expression for $v_g(t)$ we conclude $\omega = 2\pi \times 10^9$ rad/s. Therefore

$$\beta = \frac{2\pi \times 10^9 \text{ rad/s}}{3 \times 10^8 \text{ m/s}} = \frac{20\pi}{3} \text{ rad/m}$$

Then, using Eq. (2.63),

$$\begin{aligned} Z_{in} &= Z_0 \left(\frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right) \\ &= 50 \left(\frac{(100 - j100) + j50 \tan \left(\frac{20\pi}{3} \text{ rad/m} \times 5 \text{ cm} \right)}{50 + j(100 - j100) \tan \left(\frac{20\pi}{3} \text{ rad/m} \times 5 \text{ cm} \right)} \right) \\ &= 50 \left(\frac{(100 - j100) + j50 \tan \left(\frac{\pi}{3} \text{ rad} \right)}{50 + j(100 - j100) \tan \left(\frac{\pi}{3} \text{ rad} \right)} \right) = (12.5 - j12.7) \Omega \end{aligned}$$

$Z_{in}(-l) = Z_0 \left[\frac{1 + \Gamma e^{-j\beta l}}{1 - \Gamma e^{-j\beta l}} \right]$

An alternative solution to this part involves the solution to part (a) and Eq. (2.61).

(c) In phasor domain, $\tilde{V}_g = 5 \angle 0^\circ$. From Eq. (2.64), $v_g(t) = \text{Re}[\tilde{V}_g e^{j\omega t}] = 5 \cos \omega t$

$$\tilde{V}_i = \frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}} = \frac{5 \times (12.5 - j12.7)}{50 + (12.5 - j12.7)} = 1.40e^{-j34.0^\circ} \text{ (V)}$$

and also from Eq. (2.64),

$$\tilde{I}_i = \frac{\tilde{V}_i}{Z_{in}} = \frac{1.4e^{-j34.0^\circ}}{(12.5 - j12.7)} = 78.4e^{j11.5^\circ} \text{ (mA)}$$

#3

$$S = \frac{1 + |\Gamma|}{1 - |\Gamma|}, \quad \Gamma = \text{voltage reflection coef at load}$$

$$S(1 - |\Gamma|) = 1 + |\Gamma|$$

$$S = \frac{15}{5} = 3$$

$$S - S|\Gamma| = 1 + |\Gamma|$$

$$S - 1 = S|\Gamma| + |\Gamma| = |\Gamma|(1 + S)$$

$$|\Gamma| = \frac{S - 1}{S + 1} = \frac{15/5 - 1}{15/5 + 1} = \frac{3 - 1}{3 + 1} = \frac{2}{4} = \frac{1}{2}$$

Various possibilities

$$\Gamma = \frac{1}{2}, -\frac{1}{2} \text{ for a real load } z_L = R_L$$

$$|\Gamma| = \frac{1}{2}$$

for a complex or imaginary load

$$\Gamma = \pm \frac{1}{2} e^{\pm j\theta_r}, \quad |\Gamma| = \frac{1}{2}$$

for pure imaginary load

$$\theta_r = 90^\circ \quad (? \text{ see below})$$

$$\Gamma = \frac{z_L - z_0}{z_L + z_0}, \quad z_0 \text{ is real}$$



You can calculate what z_L has to be

in the cases above - if you do that, you will see that a pure imaginary load is inconsistent with $|\Gamma| = \frac{1}{2}$; if $z_L = jX$


$$|\Gamma| = \left| \frac{jX - z_0}{jX + z_0} \right| = 1, \text{ so } \theta_r \neq 90^\circ$$

is not possible

for a solution

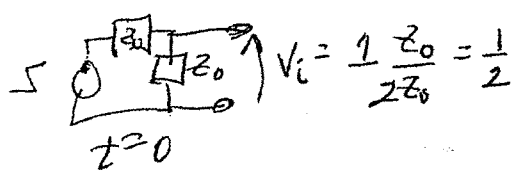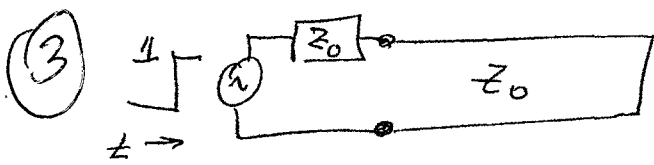

for voltage

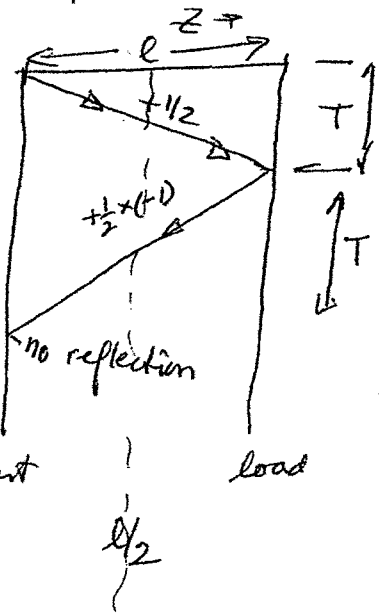

(3)



$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Gamma_L = -1 \text{ (voltage)}$$


$$\Gamma_{gen} = 0 \text{ (voltage)}$$

$\Gamma_{gen} = 0$

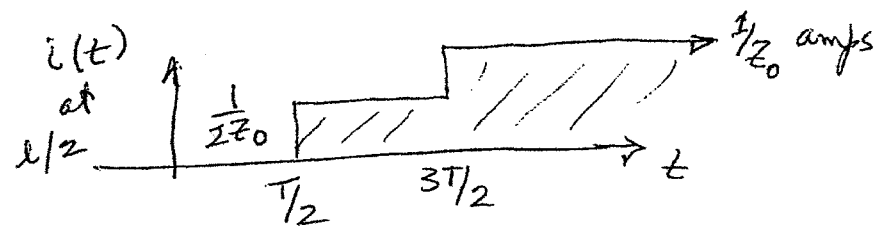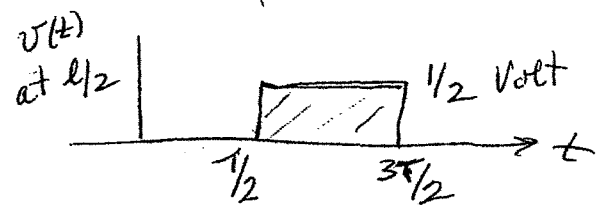
$$\left(\frac{Z_0 - Z_0}{Z_0 + Z_0} \right)$$



current

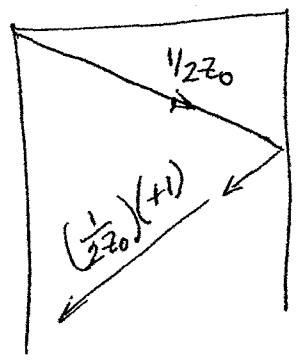


after $2T$


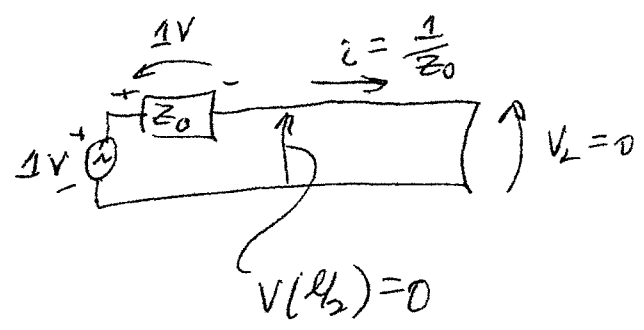


Solution to 4th problem


4

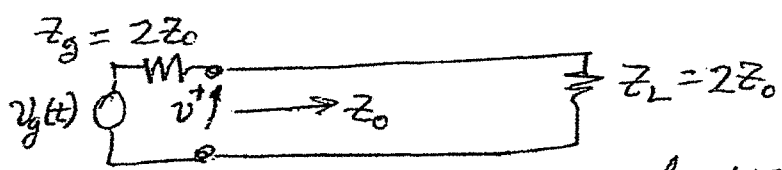

Lossless line, $z_0, \mu p = c$

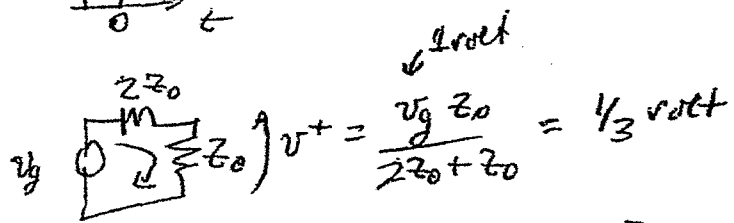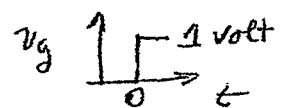

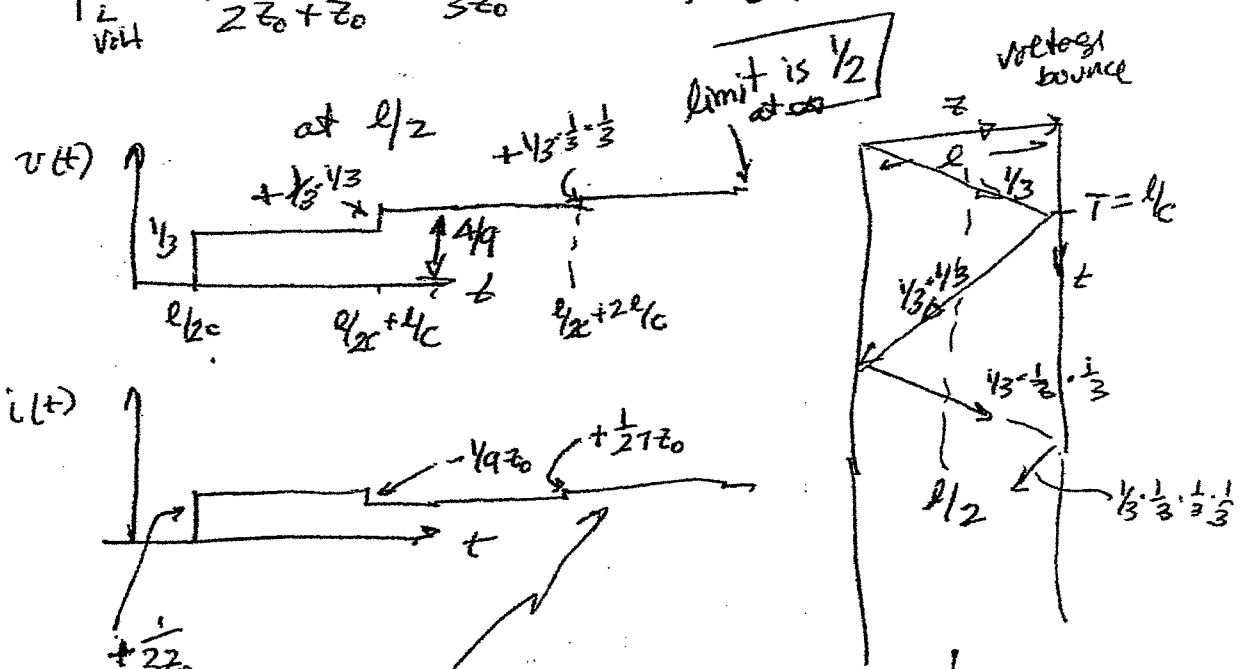$\Gamma_L = \frac{2z_0 - z_0}{2z_0 + z_0} = \frac{z_0}{3z_0} = +\frac{1}{3}$, $\Gamma_L = -\frac{1}{3}$ current



current reflections oscillate and settle at $i(t) = \frac{1}{4z_0}$

eventually $v(t)$ everywhere on the line is $1/2$, each step being $1/3$ of the previous one
 At ∞ , $v_g = 1/2$
 $i(t) = \frac{1}{4z_0}$