

SOLUTIONS : EEL 3472
TEST #1, Feb 11, 2009

Problem 1.

On this one page, describe succinctly in words and, if you wish, a few equations, the differences between a transient, time-domain solution to the transmission line equations and a phasor solution. Give a practical case for which one would need to use a time-domain solution and a case for which one would need to use a phasor solution.

The transient solution involves following in time and space a time-waveform, in our case a step function, as it reflects sequentially from each end of the line. After an ∞ number of bounces, the system settles to a dc value for the case of an input step function.

Propagating waveforms are $f(\pm \sqrt{LC}z)$, where f is any function.


The phasor solution is a steady state solution at one frequency, that is, the one-frequency generator has been "on" forever. The phasor solution handles a lossy line easier than the time domain but only at one frequency at a time. All signals are $e^{j\omega t} e^{\pm \gamma z}$, $\gamma = \alpha + j\beta$

Practical cases

Phasor: The transmission line feeding a radar antenna - one frequency, modulated some - a transmission line carries any narrow band signal
Time domain: The transmission line carrying digital signals from one place on an integrated circuit to another; a transmission line carrying any wide-band signal

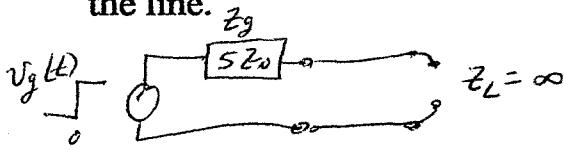Problem 2.

A unit step function is applied at $t=0$ to a lossless transmission line of length l whose characteristic impedance is Z_0 and whose Thevenin-equivalent generator impedance is $5Z_0$. The load impedance is an open circuit, $Z_L = \infty$. Plot the voltage and the current at $z=3l/4$, that is, $l/4$ from the load, from $t=0$ to $t=3T$ where $T=l/c$ and "c" is the speed of light (the speed of the voltage and current on the line). Find the voltage and current at $3l/4$ after an infinite number of reflections have occurred from both ends of the line.




$$\Gamma_{L, \text{voltage}} = \frac{\infty - Z_0}{\infty + Z_0} = +1, \quad \Gamma_{L, \text{current}} = -1$$


$$\Gamma_{g, \text{voltage}} = \frac{5Z_0 - Z_0}{5Z_0 + Z_0} = \frac{2}{3}, \quad \Gamma_{g, \text{current}} = -\frac{2}{3}$$

at $t=0$

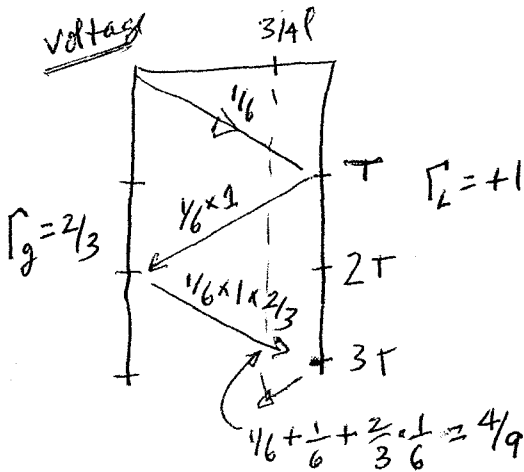
$$V_1^+ = \frac{Z_0}{6Z_0} = \frac{1}{6}, \quad I_1^+ = \frac{V_1^+}{Z_0} = \frac{1}{6Z_0}$$



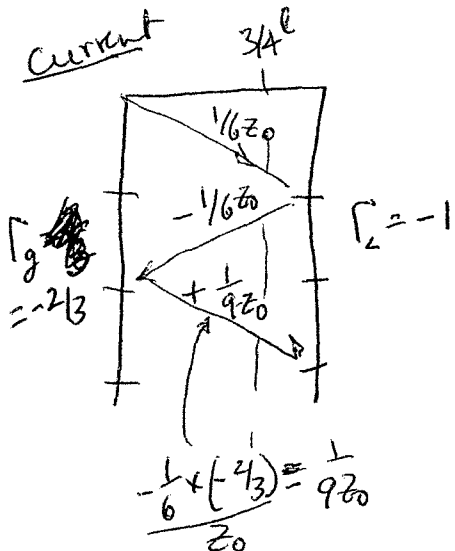when current goes to zero after an ∞ number of reflections, each smaller than the previous, the voltage at the open circuit is $v_g = 1$ via dc voltage division $V_{LOAD} = \frac{\infty}{5Z_0 + \infty} = 1$



+10
+10
+5
+5

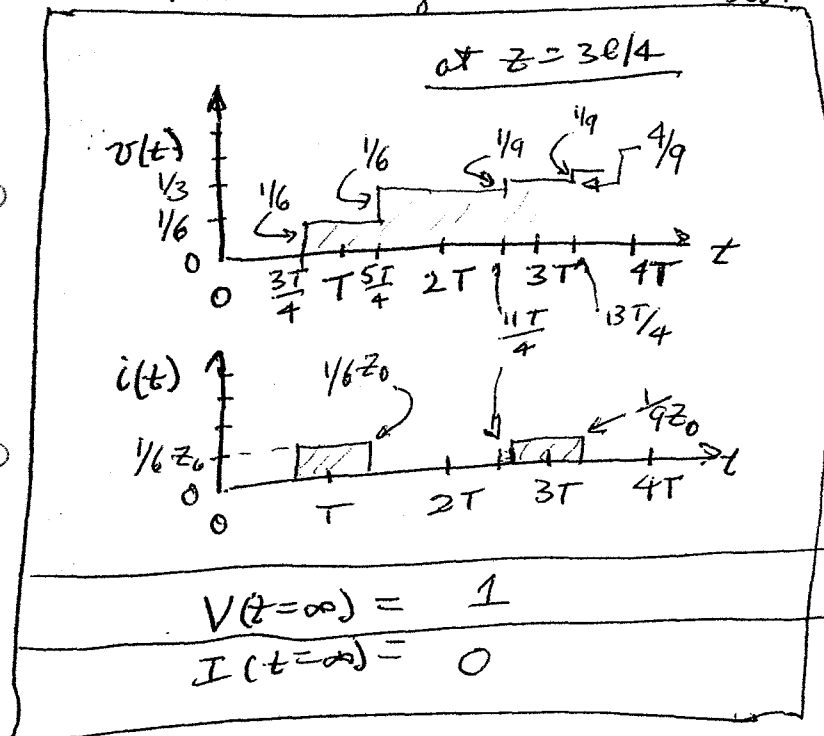

Problem 3.

A voltage generator with $v_g(t) = A \sin(2\pi \times 10^{10} t + \pi/4)$ and internal impedance 200 Ohms is connected to a lossless transmission line characterized by $L' = 10^{-6} \text{ H/m}$ and $C' = 10^{-10} \text{ F/m}$. If the load impedance is 100 Ohms and the line is 100 meters long, find:

- (a) The phasor voltage source \tilde{V}_g
- (b) The wave length λ on the line.
- (c) The propagation constant β
- (d) The voltage and current reflection coefficients at the load
- (e) The input impedance Z_m to the line
- (f) The phasor input voltage to the line \tilde{V}_i
- (g) The SWR (Standing Wave Ratio) on the line

$$Z_0 = \sqrt{\frac{L'}{C'}} = \sqrt{\frac{10^{-6}}{10^{-10}}} = 100 \Omega$$

$$u_p = \frac{1}{\sqrt{L'C'}} = \frac{1}{\sqrt{10^{-16}}} = 10^8 \text{ m/s}$$

$$\omega = 2\pi \times 10^{10} \text{ rad/s}$$

$$f = 10^{10} \text{ Hz}$$

(a) $v_g = A \sin(2\pi \times 10^{10} t + \frac{\pi}{4}) = A \cos(2\pi \times 10^{10} t + \frac{\pi}{4} - \frac{\pi}{2})$

$$\tilde{V}_g = A e^{-j\pi/4}$$

(b) $\lambda = \frac{u_p}{f} = \frac{1/\sqrt{L'C'}}{10^{10}} = \frac{10^8}{10^{10}} = 10^{-2} \text{ m}$

(c) $\beta = 2\pi/\lambda = \frac{2\pi}{10^{-2}} = 200\pi$

(d) $\Gamma_v = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{100 - 100}{100 + 100} = 0, \Gamma_i = -\Gamma_v = 0$

(e) $Z_{in}(-l) = Z_0 \left(\frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right) = Z_0 = 100 = \sqrt{\frac{L'}{C'}}$

(f) $\tilde{V}_i = \tilde{V}_g \frac{Z_m}{Z_g + Z_m} = \frac{A e^{-j\pi/4} \cdot 100}{200 + 100}$

(g) $SWR = \frac{1 + |\Gamma_v|}{1 - |\Gamma_v|} = 1$

| | |
|----|---|
| +5 | (a) $\tilde{V}_g = A e^{-j\pi/4}$ |
| +4 | (b) $\lambda = 10^{-2} \text{ m}$ |
| +4 | (c) $\beta = 200\pi$ |
| +4 | (d) $\Gamma_v = 0 \quad \Gamma_i = 0$ |
| +5 | (e) $Z_{in} = 100 \Omega$ |
| +4 | (f) $\tilde{V}_i = \frac{A}{3} e^{-j\pi/4} \text{ volts}$ |
| +4 | (g) $SWR = 1$ |